

INSTITUTE OF ENGINEERING AND TECHNOLOGY, **INDORE**



CIRCUIT DESIGN USING HDL(EIR7C4)

Lab Assignment

Session (2020-2021)

TOPIC: TWO BIT SUBTRACTOR USING STRUCTURAL FLOW

Submitted To

Dr. Vaibhav Neema

Submitted By

Akshita Ranawat
Roll No.: 17E7007
EI(7th Sem)
Enroll no. DE17199

Structural Modeling Architecture in VHDL

- ★ The term structural modeling is the terminology that VHDL uses for modular design.
- ★ If you are designing a complex project, you should split into two or more simple designs in order to easily handle the complexity. Modular designs allow you to pack low-level functionality into modules.
- ★ This approach allows design reuse without the need to reinvent and re-test the wheel every time.
- ★ We use signals to interconnect components and eventually create large systems using small sub-systems. Structural design deals with interconnection of gates, how gates are connected to each other.
- ★ Entity declaration(no need to mention Intermediate signals only input and output)
- ★ In Structural modeling, the architecture body is composed of two parts – the declarative part (before the keyword 'begin') and the statement part (after the keyword 'begin').
- ★ Component Declaration, (we define the name, Inputs/outputs, and type of Inputs/outputs of the component).
- ★ Component Instantiation

```
component label: component-name port map (  
association-list) ;
```


Two Bit Subtractor

Two bit subtractor also known as half subtractor is a combinational circuit used to perform subtraction of two bits. If it has two inputs, the minuend X and subtrahend Y and two outputs the Difference D and Borrow out B. The borrow out signal is set when the subtractor needs to borrow from the next digit. That is Borrow=1, A<B, B=1 if A=0 B=1. The logic of half subtractor looks like this,

$$DIFF = A \oplus B$$

$$Borrow = \overline{A}.B$$

Logic Diagram for Two Bit Subtractor

 

Truth Table for Two Bit Subtractor

Input A		Input B		Output DIFF		Output Borrow	
A1	A0	B1	B0	D1	D0	Br1	Br0
0	0	0	0	0	0	0	0
0	0	0	1	0	1	0	1
0	0	1	0	1	0	1	0
0	0	1	1	1	1	1	1
0	1	0	0	0	1	0	0
0	1	0	1	0	0	0	0
0	1	1	0	1	1	1	0
0	1	1	1	1	0	1	0
1	0	0	0	1	0	0	0
1	0	0	1	1	1	1	0
1	0	1	0	0	0	0	0
1	0	1	1	0	1	0	1
1	1	0	0	1	1	0	0
1	1	0	1	1	0	0	0
1	1	1	0	0	1	0	0
1	1	1	1	0	0	0	0

Test Bench for Two Bit Subtractor

testbench.vhd

VHDL Testbench

```
1 library IEEE;
2 use IEEE.STD_LOGIC_1164.ALL;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6 entity tb is
7 end entity;
8
9 architecture tb of tb is
10 component halfsubtractor is
11 port( A, B : in STD_LOGIC_VECTOR(1 downto 0);
12       DIFF : out STD_LOGIC_VECTOR(1 downto 0);
13       Borrow : out STD_LOGIC_vector(1 downto 0));
14 end component;
15
16 signal A, B, DIFF: STD_LOGIC_VECTOR(1 downto 0);
17 signal Borrow : STD_LOGIC_VECTOR(1 downto 0);
18
19 begin
20 uut: halfsubtractor port map(
21 A => A, B => B,
22 DIFF => DIFF,
23 Borrow => Borrow);
24
25 stim: process
26 begin
27
28 A <= "00";
29 B <= "00";
30 wait for 20 ns;
31
32 A <= "00";
33 B <= "01";
```



```
31
32 A <= "00";|
33 B <= "01";
34 wait for 20 ns;
35
36 A <= "00";
37 B <= "10";
38 wait for 20 ns;
39
40 A <= "00";
41 B <= "11";
42 wait for 20 ns;
43
44 A <= "01";
45 B <= "00";
46 wait for 20 ns;
47
48 A <= "01";
49 B <= "01";
50 wait for 20 ns;
51
52 A <= "01";
53 B <= "10";
54 wait for 20 ns;
55
56 A <= "01";
57 B <= "11";
58 wait for 20 ns;
59
60
61 A <= "10";
62 B <= "00";
63 wait for 20 ns;
64
.. . . .
```

testbench.vhd



VHDL Testbench

```
67 wait for 20 ns;
68
69 A <= "10";
70 B <= "10";
71 wait for 20 ns;
72
73 A <= "10";
74 B <= "11";
75 wait for 20 ns;
76
77 A <= "11";
78 B <= "00";
79 wait for 20 ns;
80
81 A <= "11";
82 B <= "01";
83 wait for 20 ns;
84
85 A <= "11";
86 B <= "10";
87 wait for 20 ns;
88
89 A <= "11";
90 B <= "11";
91 wait for 20 ns;
92
93
94 wait;
95
96 end process;
97
98 end tb;
```

VHDL Design Code for Two Bit Subtractor

design.vhd



VHDL Design

```
1  --notgate
2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4  use IEEE.STD_LOGIC_ARITH.ALL;
5  use IEEE.STD_LOGIC_UNSIGNED.ALL;
6
7  entity notgate is
8      Port ( A : in std_logic_vector(1 downto 0);
9            s : out std_logic_vector(1 downto 0));
10 end notgate;
11
12 architecture behavioural of notgate is
13 begin
14     s <= not A;
15 end behavioural;
16
17 -- andgate
18 library IEEE;
19 use IEEE.STD_LOGIC_1164.ALL;
20 use IEEE.STD_LOGIC_ARITH.ALL;
21 use IEEE.STD_LOGIC_UNSIGNED.ALL;
22
23 entity andgate is
24     Port ( B : in std_logic_vector(1 downto 0);
25           s : in std_logic_vector(1 downto 0);
26           Borrow : out std_logic_vector(1 downto 0));
27 end andgate;
28
29 architecture behavioural of andgate is
30 begin
31     Borrow <= s and B;
32 end behavioural;
33
```




```
33
34 -- xor gate
35 library IEEE;
36 use IEEE.STD_LOGIC_1164.ALL;
37 use IEEE.STD_LOGIC_ARITH.ALL;
38 use IEEE.STD_LOGIC_UNSIGNED.ALL;
39
40 entity xorgate is
41     Port ( A : in std_logic_vector(1 downto 0);
42           B : in std_logic_vector(1 downto 0);
43           DIFF : out std_logic_vector(1 downto 0));
44 end xorgate;
45
46 architecture behavioural of xorgate is
47 begin
48     DIFF <= A xor B;
49 end behavioural;
50
51
52 library IEEE;
53 use IEEE.STD_LOGIC_1164.ALL;
54 use IEEE.STD_LOGIC_ARITH.ALL;
55 use IEEE.STD_LOGIC_UNSIGNED.ALL;
56
57 entity Halfsubtractor is
58     Port ( A : in STD_LOGIC_vector(1 downto 0);
59           B : in STD_LOGIC_vector(1 downto 0);
60           DIFF : out STD_LOGIC_vector(1 downto 0);
61           Borrow : out STD_LOGIC_vector(1 downto 0));
62 end Halfsubtractor;
63 architecture Structural of Halfsubtractor is
64
65 component notgate
66     port ( A : in std_logic_vector(1 downto 0);
```




```
59         B : in  STD_LOGIC_vector(1 downto 0);
60         DIFF : out STD_LOGIC_vector(1 downto 0);
61         Borrow : out STD_LOGIC_vector(1 downto 0));
62     end Halfsubtractor;
63     architecture Structural of Halfsubtractor is
64
65     component notgate
66         port ( A : in std_logic_vector(1 downto 0);
67               s : out std_logic_vector(1 downto 0));
68     end component;
69
70     component andgate
71         port ( B : in std_logic_vector(1 downto 0);
72               s : in std_logic_vector(1 downto 0);
73               Borrow : out std_logic_vector(1 downto 0));
74     end component;
75
76     component xorgate
77         port ( A : in std_logic_vector(1 downto 0);
78               B : in std_logic_vector(1 downto 0);
79               DIFF : out std_logic_vector(1 downto 0));
80     end component;
81
82     signal s : STD_LOGIC_vector(1 downto 0) := (others => '0');
83
84     begin
85         G1: notgate port map(A,s);
86         G2: andgate port map(s,B,Borrow);
87         G3: xorgate port map(A,B,DIFF);
88     end Structural;
89
90
```

Wave Form for Two Bit Subtractor

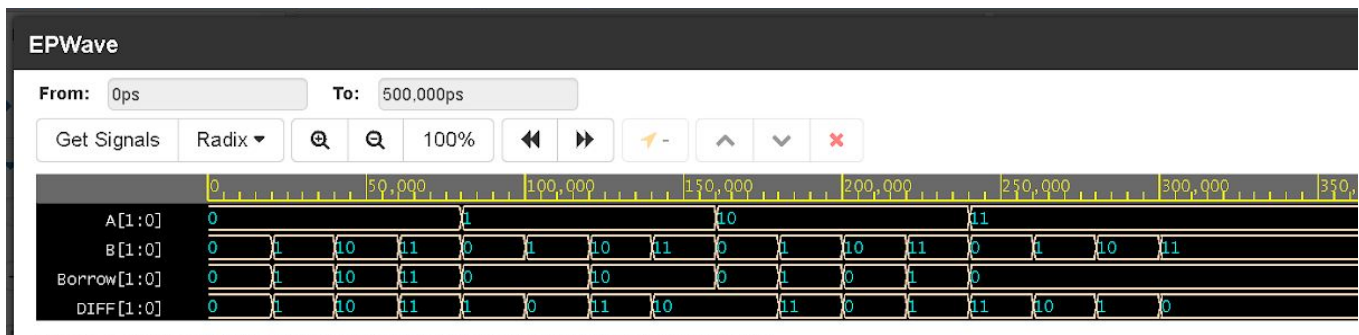

XXXXXX