

**INSTITUTE OF ENGINEERING AND TECHNOLOGY, DAVV
INDORE**



**ELECTRONICS & INSTRUMENTATION ENGINEERING
CIRCUIT DESIGN USING HDL(EIR7E1)**

LAB VIVA

Session: 2020-21

SUBMITTED TO:

Dr. Vaibhav Neema

SUBMITTED BY:

Atharva Bhanagay


Roll No: 17E7010

Email: 17bei112@ietdavv.edu.in

Phone: 9340655731



Positive Edge D Flip Flop

 The Master slave D flip flop shown below is a positive edge triggered device that means it will operate when clock input has raising edge. The first flip flop (master flip – flop) is connected with a negative clock signal i.e. Inverted and the second flip – flop (slave flip – flop) is connected with double inverse of clock signal i.e. normal clock signal.



Truth Table:

Functional Table

D	CLK	Q	QN
0		0	1
1		1	0
x	0	last Q	last QN
x	1	last Q	last QN

Design Code

```
Run Save Copy ASU students: please log on using the Google button.
design.vhd
1 Library ieee;
2 use ieee.std_logic_1164.all;
3
4 Entity ip2_nand is
5 Port ( a,b:in std_logic;
6       op:out std_logic);
7 End entity;
8
9 Architecture da of ip2_nand is
10 begin
11     Op<=a nand b;
12 End architecture;
13
14 Library ieee;
15 use ieee.std_logic_1164.all;
16
17 entity d_latch is
18 Port(clk,d:in std_logic;
19     q,qbar:out std_logic);
20 End entity;
21
22 Architecture rch of d_latch is
23 signal p1,p2,p3,q1,q2:std_logic;
24
25 component ip2_nand is
26 Port ( a,b:in std_logic;
27     op:out std_logic);
28 End component;
29 Begin
30 U1: ip2_nand port map (clk,d,p1);
31 U2: ip2_nand port map (d,d,p3);
32 U3: ip2_nand port map (clk,p3,p2);
33 U4: ip2_nand port map (p1,q2,q1);
34 U5: ip2_nand port map (q1,p2,q2);
35 q<=q1;
36 qbar<=q2;
37
38
39 Library ieee;
40 use ieee.std_logic_1164.all;
41
42 entity my_dff is
43 Port (clk,d:in std_logic;
44     q,qbar:out std_logic);
45 End entity;
46
47 Architecture rch of my_dff is
48 Signal q1,q2,q3:std_logic;
49
50 component ip2_nand is
51 Port ( a,b:in std_logic;
52     op:out std_logic);
53 End component;
54
55 component d_latch is
56 Port(clk,d:in std_logic;
57     q,qbar:out std_logic);
58 End component;
59
60 Begin
61 master : d_latch port map (q3,d,q1,q2);
62 nand4not : ip2_nand port map (clk,clk,q3);
63 slave : d_latch port map (clk,q1,q,qbar);
64 End rch;
65
66
```

Test-Bench Code

testbench.vhd



```
1 library ieee;
2 use ieee.std_logic_1164.all;
3
4 entity dff_tb is
5 end entity;
6
7 architecture tb of dff_tb is
8
9     component my_dff is
10 Port (clk,d : in std_logic;
11       q, qbar : out std_logic);
12 end component ;
13
14 signal d, clk,q, qbar : std_logic;
15
16 begin
17 dut: my_dff port map (clk,d,q,qbar);
18 Clock : process
19 begin
20 clk <= '0';
21 wait for 10 ns;
22 clk <= '1';
23 wait for 10 ns;
24 end process;
25
26 stim : process
27 begin
28
29 d <= '0';
30 wait for 29 ns;
31 d <= '1';
32 wait for 31 ns;
33 d <= '0';
34 wait for 42 ns;
35 d <= '1';
36 wait for 23 ns;
37
38 end process;
39 end tb;
```

OUTPUT Waveform



EDA Playground link:

<https://www.edaplayground.com/x/B4yA>