

INSTITUTE OF ENGINEERING AND TECHNOLOGY, DAVV , INDORE



CIRCUIT DESIGN USING HDL (EIR7C4)

LAB ASSIGNMENT

4 Bit Right Shift Register- Structural

Session 2020-2021

SUBMITTED TO :

Dr Vaibhav Neema

SUBMITTED BY :

Yug Nigam



EI, 4th year, 7th sem

(17E7061) (DE17252)

Structural Equation Modeling

Structural equation modeling is a multivariate statistical analysis technique that is used to analyze structural relationships. This technique is the combination of factor analysis and multiple regression analysis, and it is used to analyze the structural relationship between measured variables and latent constructs.

4 BIT RIGHT SHIFT USING D FLIP FLOP

 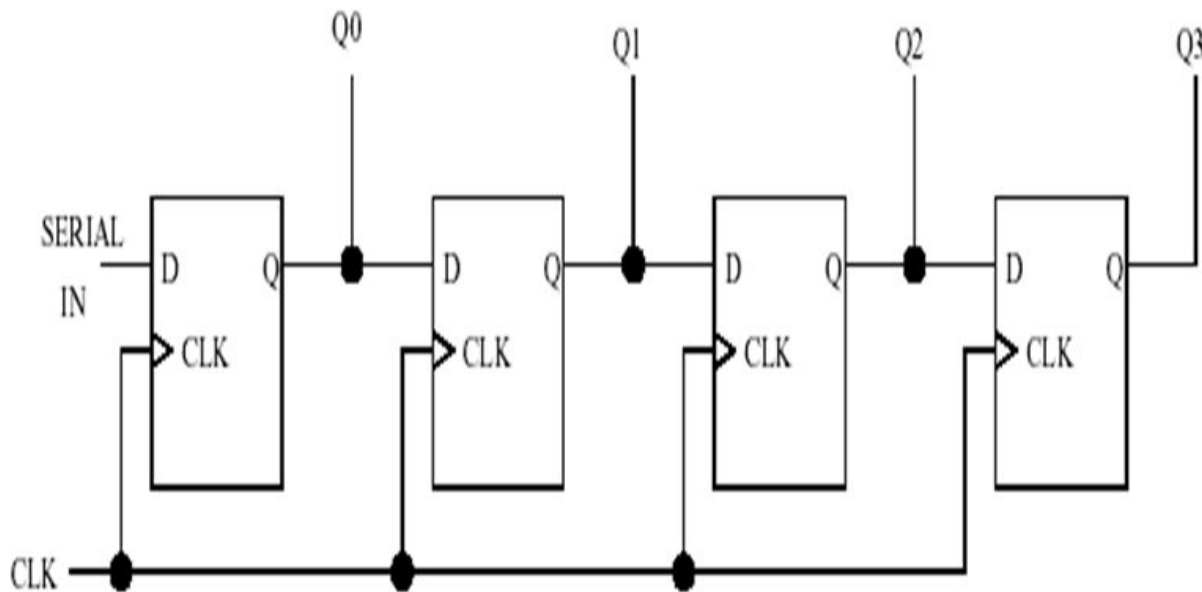

VHDL Design Code

design.vhd



```
1 library IEEE;
2 use IEEE.std_logic_1164.all;
3 use IEEE.STD_LOGIC_ARITH.ALL;
4 use IEEE.STD_LOGIC_UNSIGNED.ALL;
5
6 entity SHIFT is
7 Port ( Din,clk,reset : in STD_LOGIC;
8       Q : out STD_LOGIC_VECTOR (3 downto 0));
9 end SHIFT;
10
11 library IEEE;
12 use IEEE.std_logic_1164.all;
13 use IEEE.STD_LOGIC_ARITH.ALL;
14 use IEEE.STD_LOGIC_UNSIGNED.ALL;
15
16 entity D_FFP is
17 port( clk, reset,D: in std_logic;
18       Q: out std_logic);
19 end D_FFP;
20 architecture Behavioral of D_FFP is
21 begin
22 process(clk,reset)
23 begin
24 if(reset='1')then
25   Q <='0';
26 elsif(clk='1' and clk'event)then
27   Q <= D;
28 end if;
29 end process;
30 end Behavioral;
31
32 architecture Structural of SHIFT is
33 component D_FFP is
34 port( clk, reset,D: in std_logic;
35       Q: out std_logic);
36 end component;
37
38 signal Q_temp: std_logic_vector(3 downto 1);
39 begin
40 DFF3: D_FFP port map (clk, reset, Din, Q_temp(3));
41 DFF2: D_FFP port map (clk, reset, Q_temp(3), Q_temp(2));
42 DFF1: D_FFP port map (clk, reset, Q_temp(2), Q_temp(1));
43 DFF0: D_FFP port map (clk, reset, Q_temp(1), Q(0));
44 Q(3 downto 1)<= Q_temp;
45 end Structural;
46
```

Testbench Code

testbench.vhd



```
1  -- Code your testbench here
2  library IEEE;
3  use IEEE.std_logic_1164.all;
4  use IEEE.STD_LOGIC_ARITH.ALL;
5  use IEEE.STD_LOGIC_UNSIGNED.ALL;
6
7  ENTITY TB IS
8  END ENTITY;
9  ARCHITECTURE TB OF TB IS
10   COMPONENT SHIFT IS
11   PORT(din,clk,reset : IN std_logic;
12   Q : OUT std_logic_vector(3 downto 0));
13   END COMPONENT;
14   --Inputs
15   signal din : std_logic := '0';
16   signal clk : std_logic := '0';
17   signal reset : std_logic := '0';
18   --Outputs
19   signal Q : std_logic_vector(3 downto 0);
20 BEGIN
21   uut: SHIFT PORT MAP (din,clk,reset,Q);
22   clk_process :process
23   begin
24     clk <= '0';
25     wait for 100ns;
26     clk <= '1';
27     wait for 100ns;
28   end process;
29   stim_proc: process
30   begin
31     Reset <= '1'; Din<='1';
32     wait for 200ns;
33     Reset <= '0';
34     wait;
35   end process;
36 END;
```

EP Wave

EPWave

From: 0ps To: 1,600,000ps

Get Signals

Radix



100%

