INSTITUTE OF ENGINEERING & TECHNOLOGY INDORE



ELECTRONICS AND INSTRUMENTATION (2017-2021)

CIRCUIT DESIGN USING VHDL:


VHDL code for 4-bit Synchronous counter using data flow style of modelling

Submitted by: Shailly Shrimali Roll no. 17E7042

Email Id: 17bei142@ietdavv.edu.in

Submitted To:
Dr. Vaibhay Neema

4 bit Synchronous counter

 


VHDL Code for 4 -bit synchronous counter:

```
Testbench code:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
entity sync_counter_tb is
end entity;
architecture tb of sync_counter_tb is
component updown_count is
Port ( clk,rst,updown : in STD_LOGIC;
count : out STD_LOGIC_VECTOR (3 downto 0));
end component;
signal clk, rst, updown: STD_LOGIC:= '0';
signal count: STD_LOGIC_VECTOR (3 downto 0);
constant num_of_clocks : integer := 20;
signal i : integer := 0;
constant T: time := 20 ns;
begin
uut: updown_count port map(
clk => clk,
rst => rst,
updown => updown,
```

```
count => count);
process
begin
rst <= '0';
clk <= '0';
wait for T/2;
clk <= '1';
wait for T/2;
if (i = num_of_clocks) then
wait;
else
i <= i + 1;
end if;
if (i < 10) then
updown <= '0';
else
updown <= '1';
end if;
end process;
end tb;
Design code:
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity updown_count is
  Port ( clk,rst,updown : in STD_LOGIC;
     count : out STD_LOGIC_VECTOR (3 downto 0));
end updown_count;
architecture Behavioral of updown_count is
signal temp:std_logic_vector(3 downto 0):="0000";
begin
process(clk,rst)
begin
if(rst='1')then
temp<="0000";
elsif(rising_edge(clk))then
if(updown='0')then
temp<=temp+1;
else
temp<=temp-1;
end if;
end if;
end process;
count<=temp;</pre>
end Behavioral;
```

Waveform:

 

The above VHDL can be viewed here: https://www.edaplayground.com/x/Ki_f