

# **INSTITUTE OF ENGINEERING AND TECHNOLOGY**

## **DAVV , INDORE**



### **CIRCUIT DESIGN USING HDL (EIR7C4)**

**(Lab Assignment)**

**Session (2020-21)**

**Submitted to:-**


Dr. Vaibhav Nema

**Submitted by :-**


Name:- Rahul Patel

Roll. No:-17E7033

 **1:8 demux using structural modeling :-**



**Circuit diagram:-**

 

### Truth table:-

S2	S1	S0	O0	O1	O2	O3	O4	O5	O6	O7
0	0	0	I	0	0	0	0	0	0	0
0	0	1	0	I	0	0	0	0	0	0
0	1	0	0	0	I	0	0	0	0	0
0	1	1	0	0	0	I	0	0	0	0
1	0	0	0	0	0	0	I	0	0	0
1	0	1	0	0	0	0	0	I	0	0
1	1	0	0	0	0	0	0	0	I	0
1	1	1	0	0	0	0	0	0	0	I

### Design code:-

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL;
```

```
entity demuxstu is
```

```
    Port ( din : in STD_LOGIC;
```

```
          s : in STD_LOGIC_VECTOR (2 downto 0);
```

```
          y : out STD_LOGIC_VECTOR (7 downto 0) );
```

```
end demuxstu;
```

```
architecture structural of demuxstu is
```

```
    component notgate
```

```
        Port ( a : in STD_LOGIC;
```

```
              b : out STD_LOGIC) ;
```

```
    end component;
```

```
    component andgate is
```

```

Port ( a,b,c,d : in STD_LOGIC;
      e : out STD_LOGIC);
end component;
signal s2b, s1b, s0b:std_logic;
begin
z1:notgate port map (s(2), s2b);
z2:notgate port map (s(1), s1b) ;
z3:notgate port map (s(0), s0b) ;
z4:andgate port map (s2b, s1b, s0b, din, y (0));
z5:andgate port map (s2b, s1b, s(0), din, y(1) );
z6: andgate port map (s2b, s(1), s0b, din, y (2));
z7: andgate port map (s2b, s(1),s (0),din, y (3));
z8: andgate port map (s(2), s1b,s0b,din, y(4));
z9: andgate port map (s(2), s1b,s (0), din,y(5));
z10: andgate port map (s(2),s(1), s0b, din, y(6));
z11:andgate port map (s(2),s (1),s(0), din,y(7));
end structural ;

```

### **Test bench:-**

```

library IEEE;
use IEEE.std_logic_1164.all;
entity demux_tb is
end entity;
architecture demux1_8 of demux_tb is
component dmux1_8 is

```

```

port( din : in STD_LOGIC;
      s : in STD_LOGIC_VECTOR (2 downto 0);
      y : out STD_LOGIC_VECTOR (7 downto 0));
end component;

signal din : STD_LOGIC;
signal s: STD_LOGIC_VECTOR (2 downto 0);
signal y: STD_LOGIC_VECTOR (7 downto 0);
begin
  uut: dmux1_8 port map(    din => din,
    s => s,
    y => y);
  stim: process
  begin
    din <= '1';
    s <= "000";  wait for 20 ns;
    s <= "001";  wait for 20 ns;
    s <= "010";  wait for 20 ns;
    s <= "011";  wait for 20 ns;
    s <= "100";  wait for 20 ns;
    s <= "101";  wait for 20 ns;
    s <= "110";  wait for 20 ns;
    s <= "111";  wait for 20 ns;
    wait;
  end process;
end demux1_8;

```

## Output wave:-

