

# INSTITUTE OF ENGINEERING AND TECHNOLOGY, INDORE




## EIR7E1: Circuit Design Using HDL "Designing 8:3 encoder on VHDL"

Submitted to:  
Dr. Vaibhav Neema

Submitted By:  
Parag Nainani  
17E7029
 
## 8:3 Encoder

The 8 to 3 Encoder or octal to Binary encoder consists of **8 inputs**: Y7 to Y0 and **3 outputs**: A2, A1 & A0. Each input line corresponds to each octal digit and three outputs generate corresponding binary code.



### Truth Table for 8:3 encoder

INPUTS								OUTPUTS		
Y7	Y6	Y5	Y4	Y3	Y2	Y1	Y0	A2	A1	A0
0	0	0	0	0	0	0	1	0	0	0
0	0	0	0	0	0	1	0	0	0	1
0	0	0	0	0	1	0	0	0	1	0
0	0	0	0	1	0	0	0	0	1	1
0	0	0	1	0	0	0	0	1	0	0
0	0	1	0	0	0	0	0	1	0	1
0	1	0	0	0	0	0	0	1	1	0
1	0	0	0	0	0	0	0	1	1	1


**Boolean Equation for the outputs A0, A1 and A2 can be given as:**

$$A2 = Y7 + Y6 + Y5 + Y4$$

$$A1 = Y7 + Y6 + Y3 + Y1$$

$$A0 = Y7 + Y5 + Y3 + Y1$$

 These Equations can be implemented using 4-input OR gates



# VHDL Code to implement 8:3 Encoder using Dataflow Method

## DESIGN CODE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity ENCODER_SOURCE is
    Port (Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7 : in STD_LOGIC;
          A0,A1,A2 : out STD_LOGIC);
end ENCODER_SOURCE;

architecture dataflow of ENCODER_SOURCE is
begin

    A2 <= Y7 OR Y6 OR Y5 OR Y4;
    A1 <= Y7 OR Y6 OR Y3 OR Y2;
    A0 <= Y7 OR Y5 OR Y3 OR Y1;

end dataflow;
```

## TESTBENCH CODE

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity encoder_dataflow_tb is
end entity;

architecture encoder_dataflow_tb of encoder_dataflow_tb is
component ENCODER_SOURCE is
Port ( Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7 : in STD_LOGIC;
A0,A1,A2 : out STD_LOGIC);
end component;

signal Y0,Y1,Y2,Y3,Y4,Y5,Y6,Y7, A0, A1 ,A2: STD_LOGIC;
begin
uut: ENCODER_SOURCE port map(
Y0 => Y0, Y1 => Y1,
Y2 => Y2, Y3 => Y3,
Y4 => Y4, Y5 => Y5,
Y6 => Y6, Y7 => Y7,
A2 => A2, A1=>A1, A0=> A0);

stim: process
begin
Y7 <= '0';
```

```
Y6 <= '0';  
Y5 <= '0';  
Y4 <= '0';  
Y3 <= '0';  
Y2 <= '0';  
Y1 <= '0';  
Y0 <= '1';  
wait for 20 ns;
```

```
Y7 <= '0';  
Y6 <= '0';  
Y5 <= '0';  
Y4 <= '0';  
Y3 <= '0';  
Y2 <= '0';  
Y1 <= '1';  
Y0 <= '0';  
wait for 20 ns;
```

```
Y7 <= '0';  
Y6 <= '0';  
Y5 <= '0';  
Y4 <= '0';  
Y3 <= '0';  
Y2 <= '1';  
Y1 <= '0';  
Y0 <= '0';
```

wait for 20 ns;

Y7 <= '0';

Y6 <= '0';

Y5 <= '0';

Y4 <= '0';

Y3 <= '1';

Y2 <= '0';

Y1 <= '0';

Y0 <= '0';

wait for 20 ns;

Y7 <= '0';

Y6 <= '0';

Y5 <= '0';

Y4 <= '1';

Y3 <= '0';

Y2 <= '0';

Y1 <= '0';

Y0 <= '0';

wait for 20 ns;

Y7 <= '0';

Y6 <= '0';

Y5 <= '1';

Y4 <= '0';

Y3 <= '0';


```
Y2 <= '0';  
Y1 <= '0';  
Y0 <= '0';  
wait for 20 ns;
```

```
Y7 <= '0';  
Y6 <= '1';  
Y5 <= '0';  
Y4 <= '0';  
Y3 <= '0';  
Y2 <= '0';  
Y1 <= '0';  
Y0 <= '0';  
wait for 20 ns;
```

```
Y7 <= '1';  
Y6 <= '0';  
Y5 <= '0';  
Y4 <= '0';  
Y3 <= '0';  
Y2 <= '0';  
Y1 <= '0';  
Y0 <= '0';  
wait for 20 ns;  
wait;  
end process;  
end encoder_dataflow_tb;
```



# SIMULATION WAVEFORM

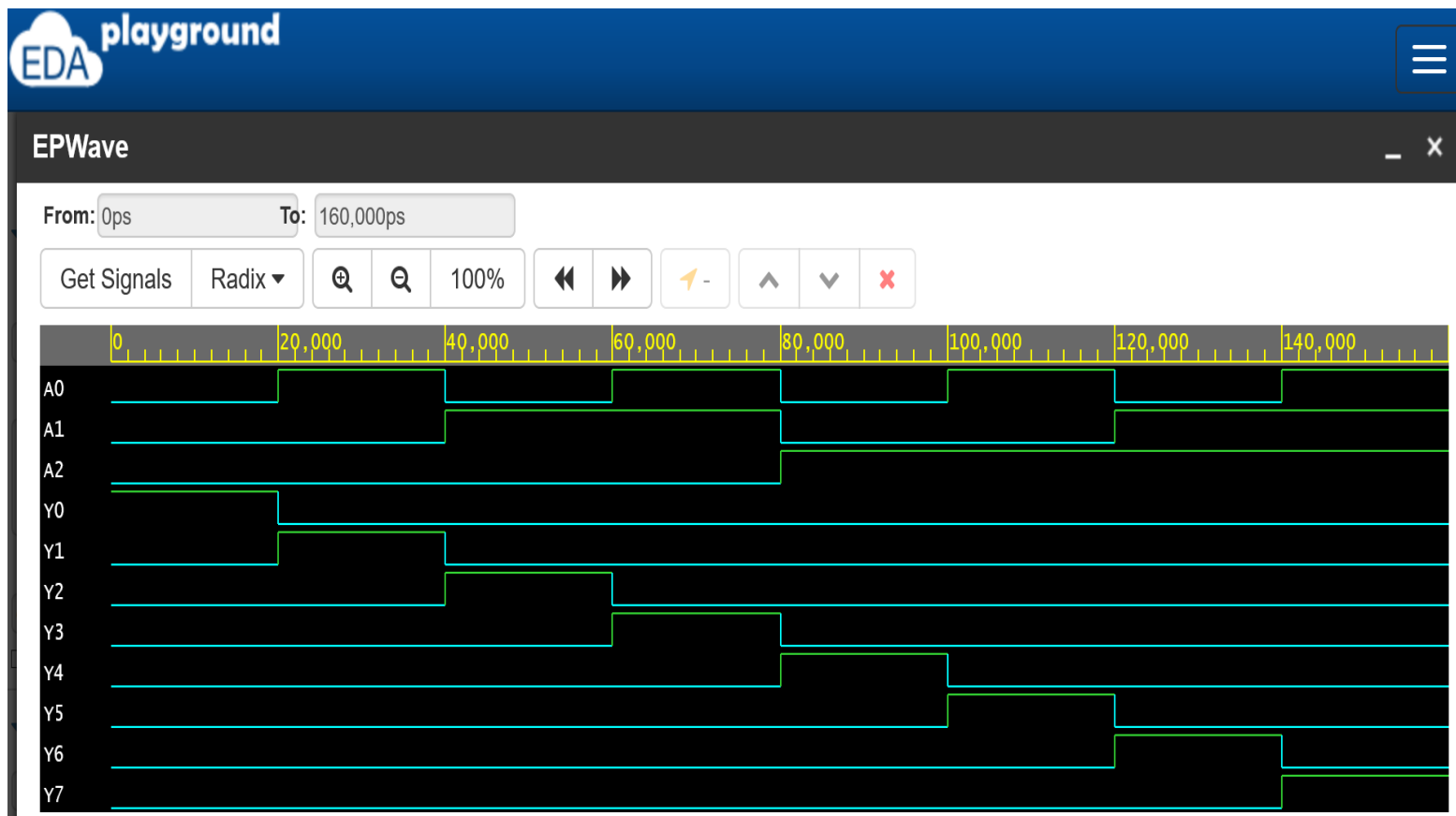

You can visit this website to view my code  
and also run the simulation:

<https://www.edaplayground.com/x/MwSg>