

**INSTITUTE OF ENGINEERING AND TECHNOLOGY, DAVV  
INDORE**



**ELECTRONICS & INSTRUMENTATION ENGINEERING  
CIRCUIT DESIGN USING HDL(EIR7E1)**

**LAB VIVA**

**Session: 2020-21**

**SUBMITTED TO:**

Dr. Vaibhav Neema

**SUBMITTED BY:**


Sarthak Kanojiya

Roll No: 17E7041

Email: [kanojiyasarthak8@gmail.com](mailto:kanojiyasarthak8@gmail.com)

Phone: 9669290976

# 4x1 Multiplexer

 

## Truth table of a 4:1 Mux

Selection Lines		Output
$s_1$	$s_0$	$Y$
0	0	$I_0$
0	1	$I_1$
1	0	$I_2$
1	1	$I_3$

# Design code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity MUX4_1 is
    Port ( i : in  STD_LOGIC_VECTOR (3 downto 0);
          s : in  STD_LOGIC_VECTOR (1 downto 0);
          y : out  STD_LOGIC);
end MUX4_1;

architecture dataflow of MUX4_1 is

begin

with s select
y <=      i(0) when "00",
          i(1) when "01",
          i(2) when "10",
          i(3) when others;

end dataflow;
```

# Test-bench code

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux4_1_tb is
end entity;

architecture tb of Mux4_1_tb is
    component MUX4_1 is
        Port ( i : in STD_LOGIC_VECTOR (3 downto 0);
              s : in STD_LOGIC_VECTOR (1 downto 0);
              y : out STD_LOGIC);
    end component;

    signal i : STD_LOGIC_VECTOR (3 downto 0);
    signal s : STD_LOGIC_VECTOR (1 downto 0);
    signal y : STD_LOGIC;

begin

    uut: MUX4_1 port map(
        i => i,
        s => s,
        y => y);

    stim: process
    begin

        i <= "1010";

        s <= "00";
        wait for 20 ns;


        s <= "01";
        wait for 20 ns;

        s <= "10";
        wait for 20 ns;

        s <= "11";
        wait for 20 ns;
        wait;

    end process;
end tb;
```

# Output Waveform:

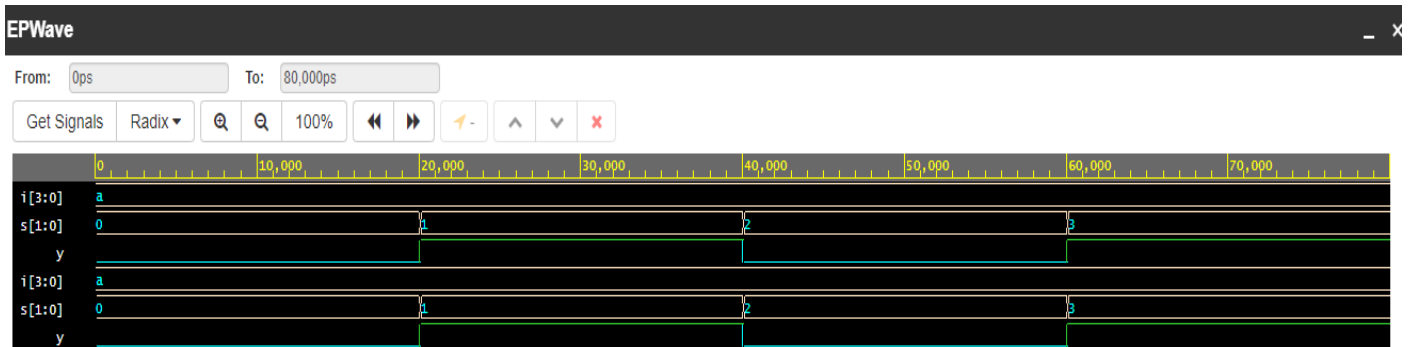

Eda playground link:

<https://www.edaplayground.com/x/H25z>